
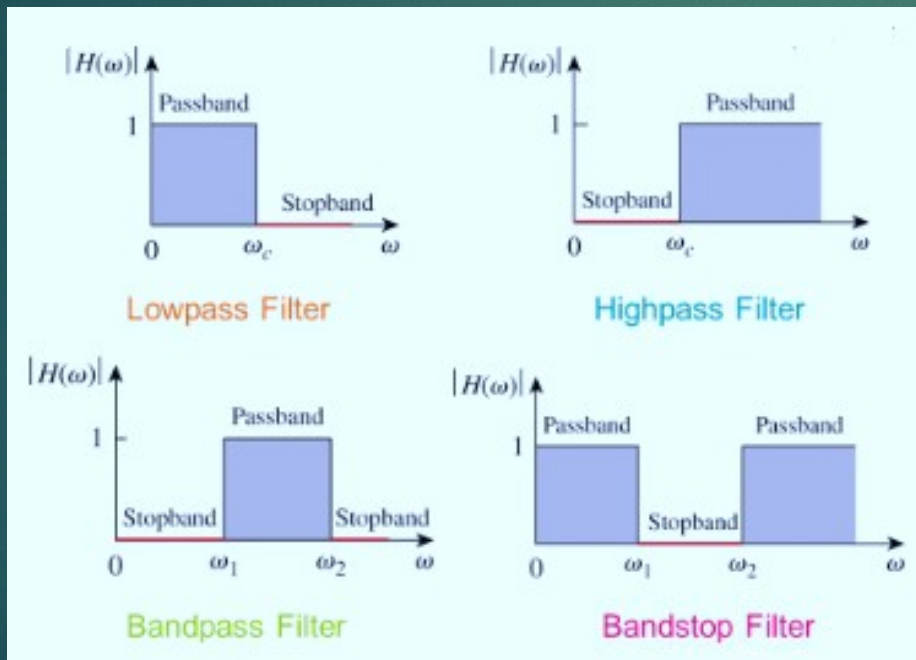


# Active Filters

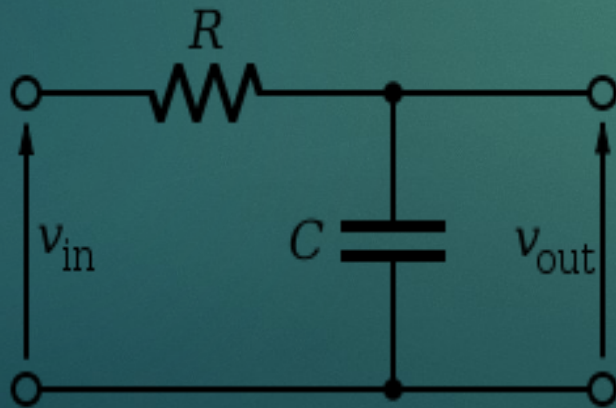


# Filters

- ▶ A filter is a circuit capable of passing (or amplifying) certain frequency signals while attenuating other frequency signals.
- ▶ The filters are divided based on the components used while designing the filters.
- ▶ If the design of the filter is completely based on passive components then the filter is called passive filter.
- ▶ On the other hand, if we use an active component (op-amp, voltage source, current source) while designing a circuit then the filter is called an active filter.




**Passive Filter**

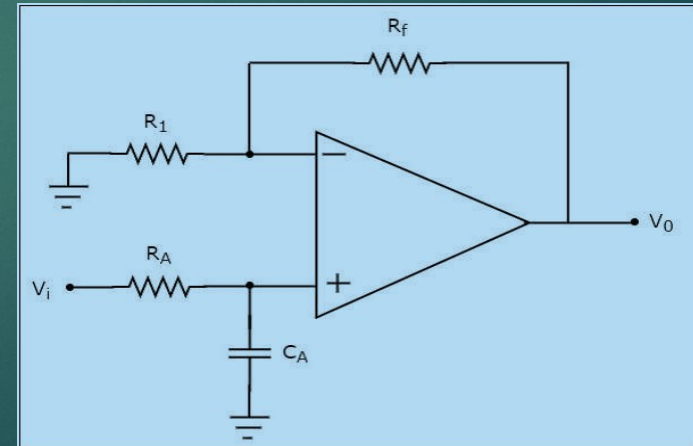


**Active Filter**


# Filter Response

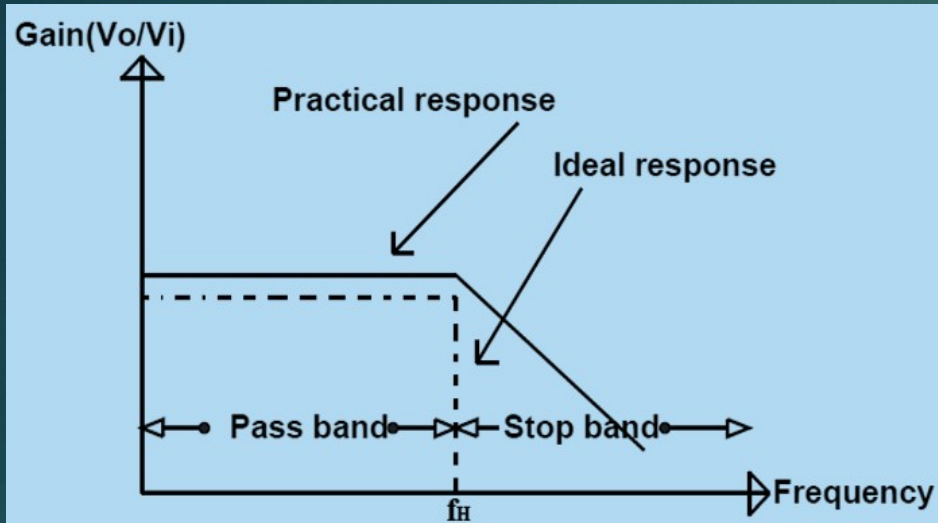

**Low Pass Filter**

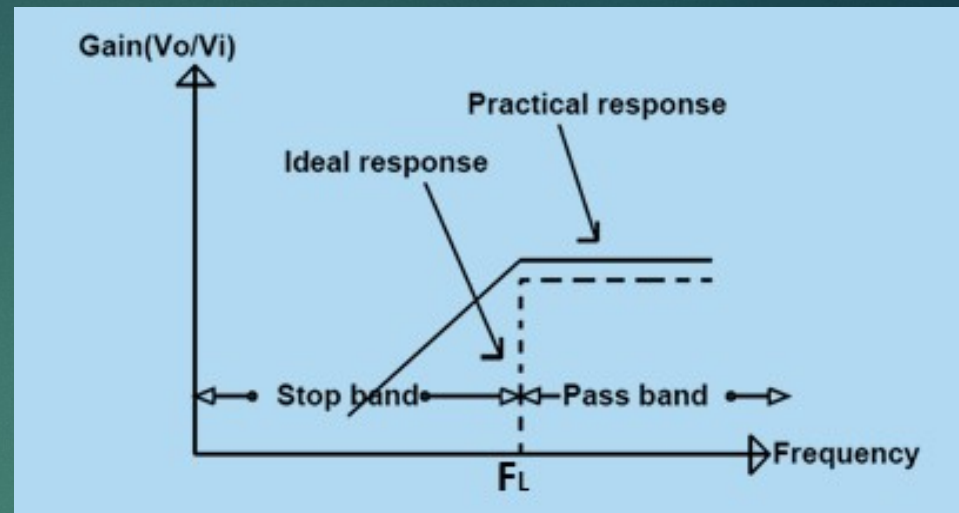

**High Pass Filter**


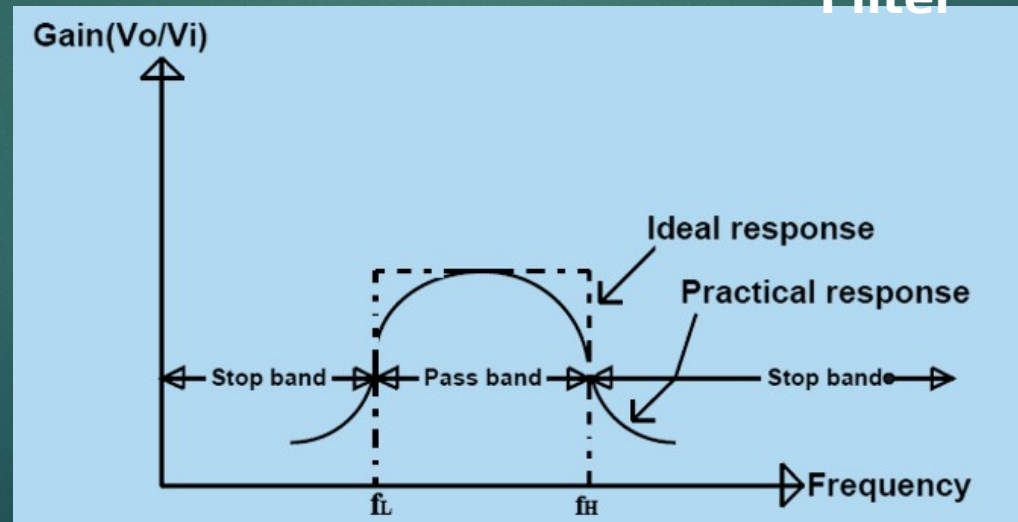


**Band Pass Filter**



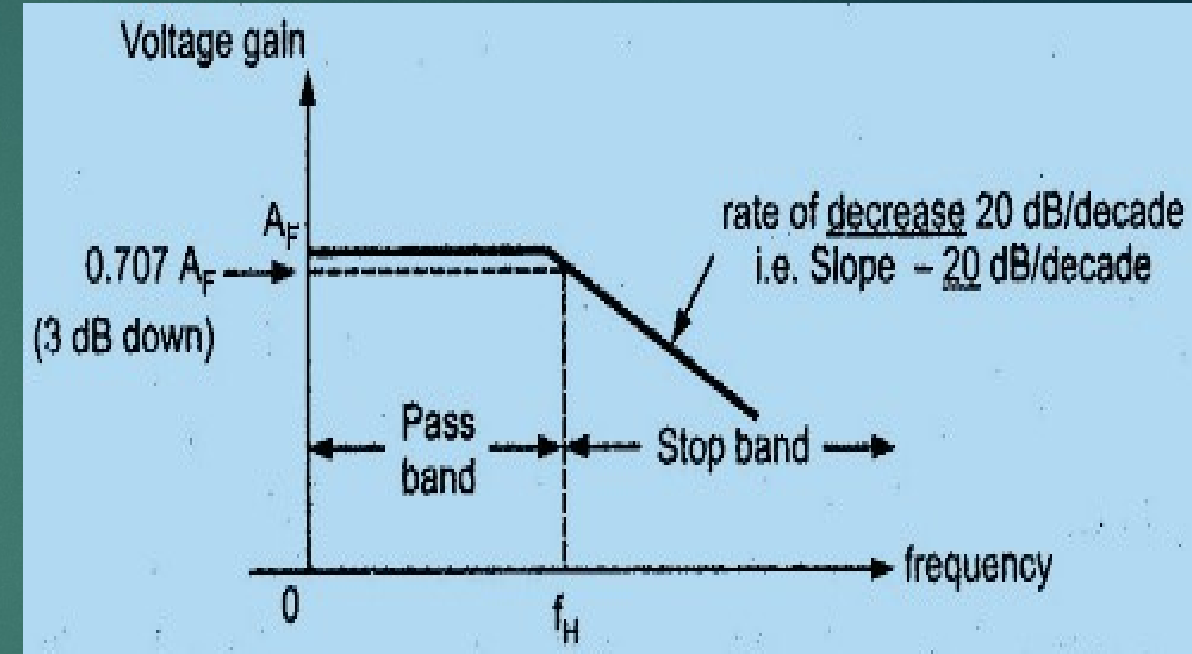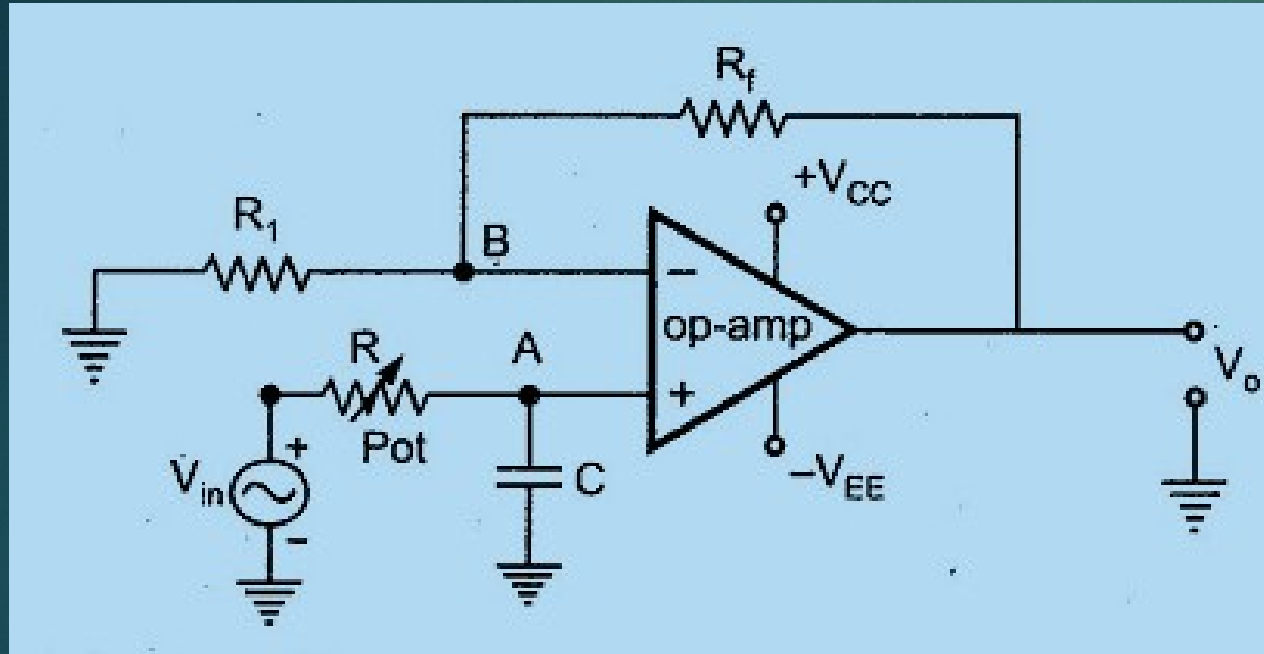
# First Order Low Pass Butterworth Filter

A low pass filter will pass low frequency signals while attenuating the high frequency signals.



The range of frequencies for which a filter does not cause significant attenuation is called the **passband**, and the range of frequencies for which the filter does cause significant attenuation is called the **stopband**.

# Continued

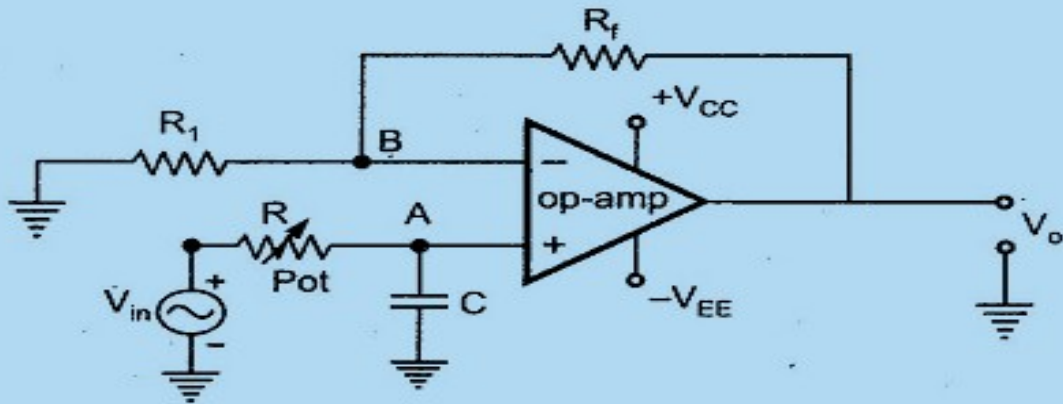

By potential divider rule, the voltage at the noninverting input terminal A which is the voltage across capacitor C is given by:

$$V_A = \frac{-jX_C}{R - jX_C} \cdot V_{in} \quad \dots (1)$$

$$\begin{aligned} V_A &= \frac{-j\left(\frac{1}{2\pi fC}\right)}{R - j\left(\frac{1}{2\pi fC}\right)} \cdot V_{in} = \frac{-j}{2\pi fRC - j} \cdot V_{in} \\ &= \frac{V_{in}}{1 - \frac{2\pi fRC}{j}} \end{aligned}$$

$$-j = \frac{1}{j} \quad \text{and} \quad -\frac{1}{j} = j$$

$$V_A = \frac{V_{in}}{1 + j2\pi fRC} \quad \dots (2)$$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_A \quad \dots (3)$$

$$\begin{aligned} V_o &\approx \left(1 + \frac{R_f}{R_1}\right) \frac{V_{in}}{(1 + j2\pi fRC)} \\ \frac{V_o}{V_{in}} &\approx \frac{A_f}{1 + j\left(\frac{f}{f_H}\right)} \end{aligned} \quad (4)$$

$$A_f = \left(1 + \frac{R_f}{R_1}\right) = \text{gain of filter in pass band} \quad \dots (5)$$

$$f_H = \frac{1}{2\pi RC} = \text{high cut off frequency of filter} \quad \dots (6)$$

$f$  = operating frequency

# Continued

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + \left( \frac{f}{f_H} \right)^2}}$$

1. At very low frequencies,  $f < f_H$


$$\left| \frac{V_o}{V_{in}} \right| \cong A_F \text{ i.e. constant}$$

2. At  $f = f_H$ ,

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{2}} = 0.707 A_F \text{ i.e. 3 dB down to the level of } A_F.$$

3. At  $f > f_H$

$$\left| \frac{V_o}{V_{in}} \right| < A_F$$

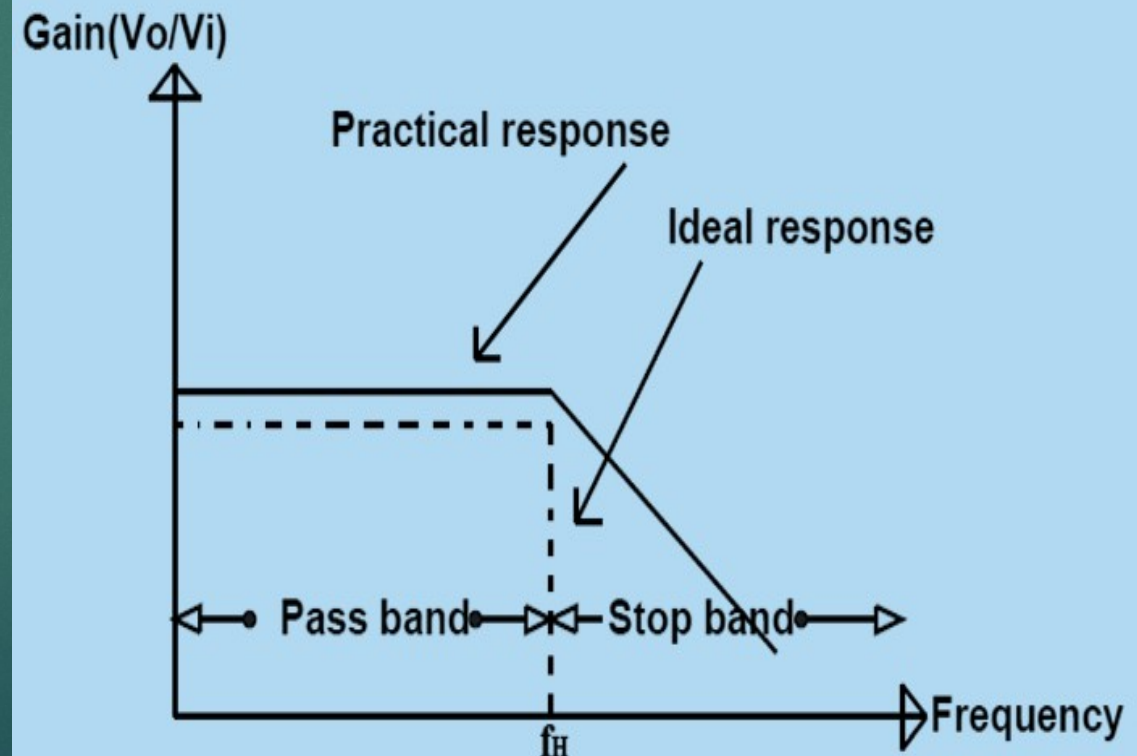



# Filter Design Steps



## Design Steps

The design steps for the first order low pass Butterworth filter are

- 1) Choose the cut off frequency,  $f_H$ .
- 2) Choose the capacitance  $C$  usually between 0.001 and 1  $\mu\text{F}$ . Generally, it is selected as 1  $\mu\text{F}$  or less than that. For better performance, mylar or tantalum capacitors are selected.
- 3) Now, for the RC circuit,

$$f_H = \frac{1}{2\pi RC}$$

Hence, as  $f_H$  and  $C$  are known, calculate the value of  $R$ .


- 4) The resistances  $R_f$  and  $R_1$  can be selected depending on the required gain in the pass band.

$$A_F = 1 + \frac{R_f}{R_1}$$

Example: Design a non-inverting active low pass filter circuit that has a gain of ten at low frequencies, a high frequency cut-off or corner frequency of 159Hz and an input impedance of 10K $\Omega$ .
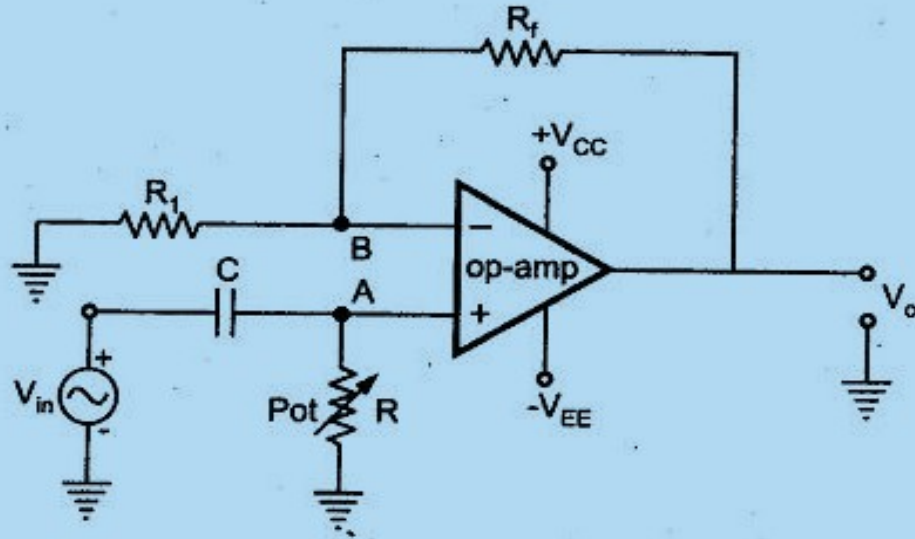
# First Order High Pass Butterworth Filter

A high pass filter that will pass the high frequency signals while attenuating the low frequency signals.



For the first order high pass filter, the output voltage is

$$V_o = \left(1 + \frac{R_F}{R_1}\right) \times \left(\frac{j2\pi f RC}{1 + j2\pi f RC}\right) \times V_{in}$$


$$\frac{V_o}{V_{in}} = A_F \times \left(\frac{j(f/f_L)}{1 + j(f/f_L)}\right)$$

where

$A_F = 1 + R_F/R_1$  — pass band gain of the filter

$f$  = frequency of the input signal

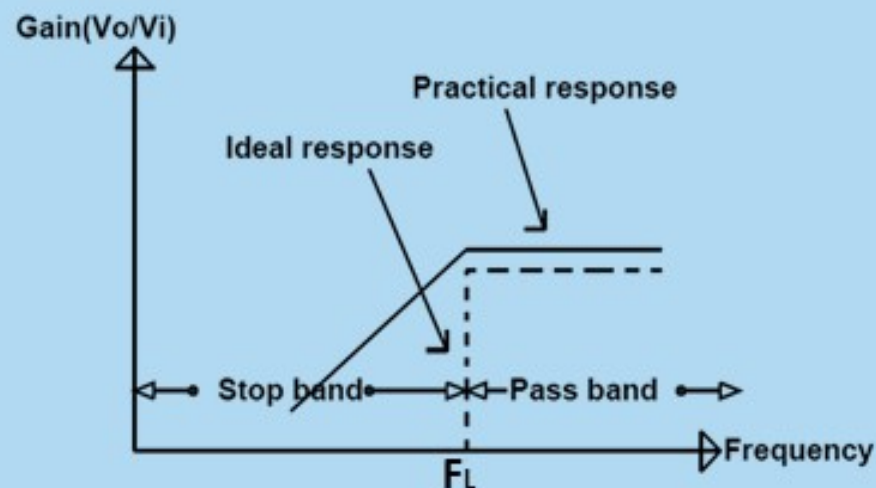$f_L = 1/(2\pi RC)$  — low cutoff frequency.




Hence the magnitude of the voltage gain is

$$\left|\frac{V_o}{V_{in}}\right| = \frac{A_F(f/f_L)}{\sqrt{1 + (f/f_L)^2}}$$


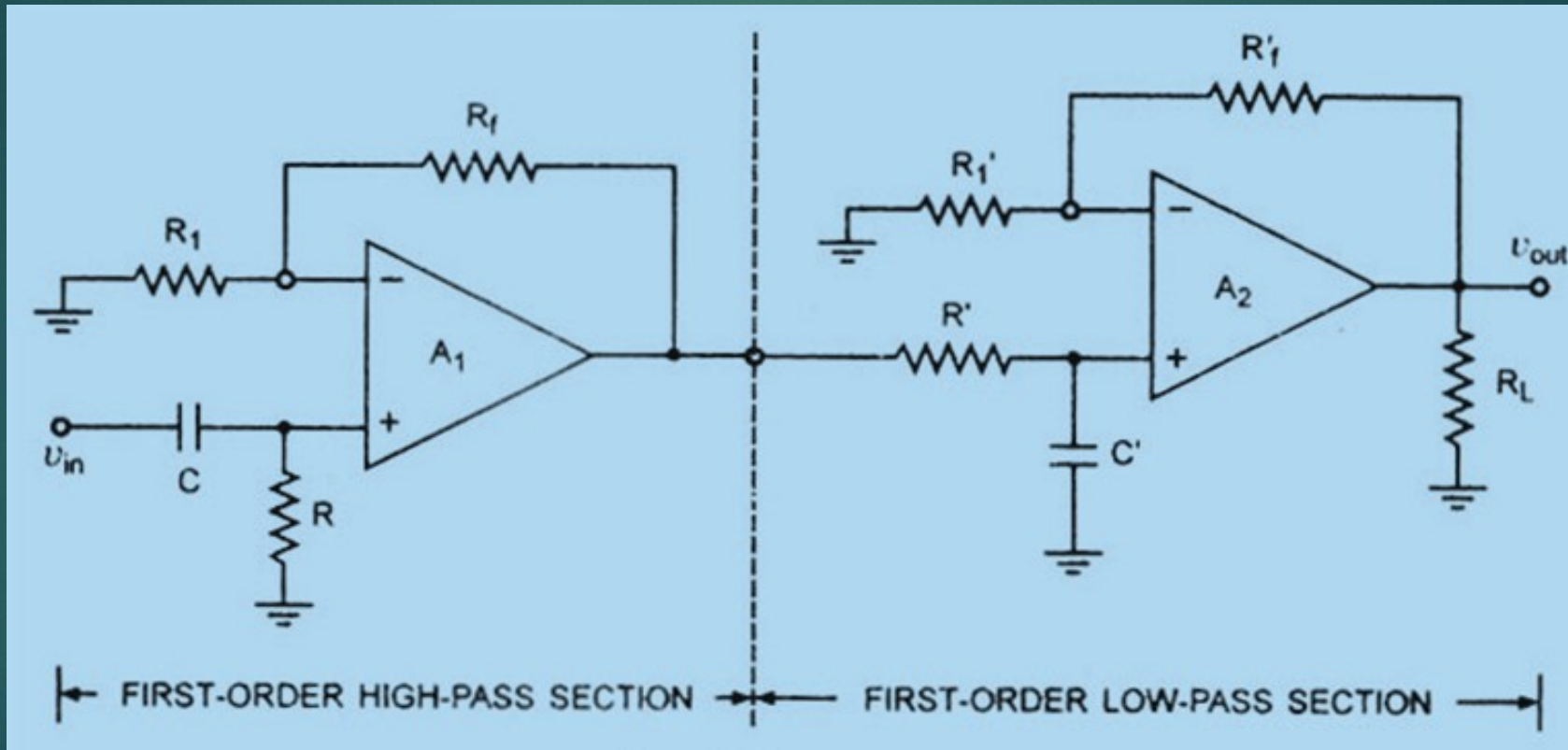
# Band Pass Filter

- ▶ A band-pass filter is a circuit which is designed to pass signals only in a certain band of frequencies while attenuating all signals outside this band.



# CONTINUED

- ▶ The parameters of importance in a bandpass filter are the high and low cut-off frequencies ( $f_H$  and  $f_L$ ), the bandwidth (BW), the centre frequency  $f_c$ , centre-frequency gain, and the selectivity or Q.
- ▶ **There are basically two types of bandpass filters viz wide bandpass and narrow bandpass filters.**
- ▶ A bandpass filter is defined as a wide bandpass if its figure of merit or quality factor Q is less than 10 while the bandpass **filters with  $Q > 10$  are called the narrow bandpass filters.**
- ▶ Thus Q is a measure of selectivity, meaning the higher the value of Q the more selective is the filter, or the narrower is the bandwidth (BW).

$$Q = \frac{f_c}{BW} = \frac{f_c}{f_H - f_L}$$


For the wide band-pass filter the center frequency  $f_c$  can be defined as

$$f_c = \sqrt{f_H f_L}$$

where  $f_H$  = high cutoff frequency (Hz)

$f_L$  = low cutoff frequency of the wide band-pass filter (Hz)

# Continued

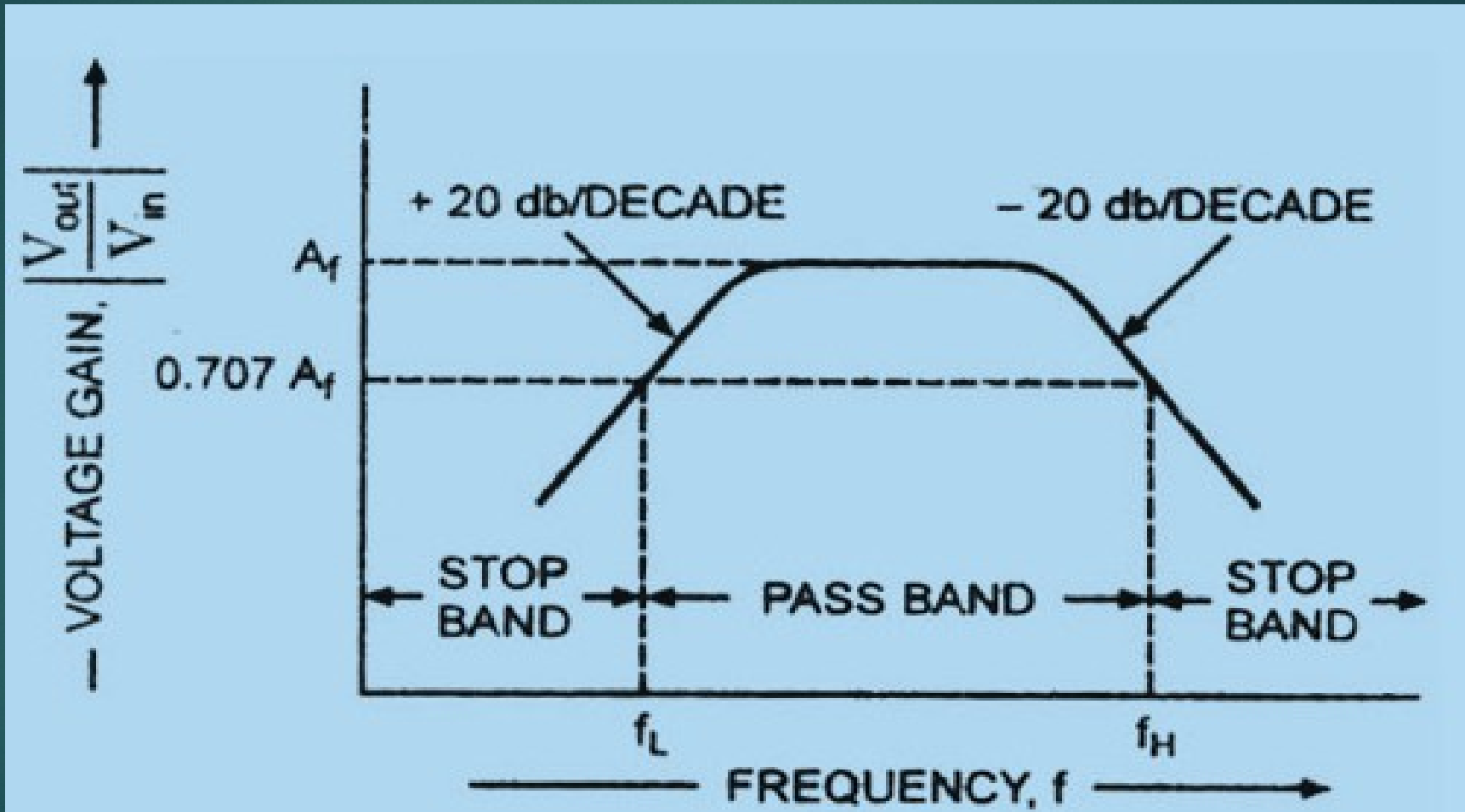





**Thank you**